

Booth Multiplier

Syomantak Chaudhuri

170070004

April 2019

1 Algorithm

This algorithm focuses on trying to multiply two bits of multiplier at a time rather than the conventional 1 bit at a time approach. Consider multiplication $A \times B$. If we encounter 00 in multiplier, then the result is 0. If we encounter 01 then results is A . If we encounter 10 then results is $2A$. If we encounter 11 then results is $3A$. A and $2A$ are easily obtained but for $3A$ we use a smart approach. Since, $3A = 4A - A$, subtract A at this stage and tell the next stage to add $4A$. Since the next stage is already 2 position ahead of this, we only need to add an extra A . To make the logic simpler, we write $2A$ as $4A - 2A$ and subtract $2A$ whenever we encounter 10 in multiplier.

So what I described above did not consider the 'carry' of A from previous sub-part of the multiplier. Taking that into account, if we encounter say 10 in B and previous bit is 1 then we know we need to add A at this position (previous bit 1 means either 10 or 11 previously - in both cases we add $4A$ which is equivalent to adding A at this shifted position). 10 also means $4A - 2A$, therefore, at this position I need to do $A - 2A = -A$ and the next part would take care of the $4A$. In this fashion, the following table is constructed:

| Current Bits (X) | Previous Bit (Y) | Increment due to X | Increment due to Y | Net change |
|---------------------|---------------------|--------------------|--------------------|------------|
| 00 | 0 | 0 | 0 | 0 |
| 00 | 1 | 0 | A | A |
| 01 | 0 | A | 0 | A |
| 01 | 1 | A | A | $2A$ |
| 10 | 0 | $-2A$ | 0 | $-2A$ |
| 10 | 1 | $-2A$ | A | $-A$ |
| 11 | 0 | $-A$ | 0 | $-A$ |
| 11 | 1 | $-A$ | A | 0 |

Table 1: Increment rule


2 Components




- 8 MUX-2 input
- 32 NOT gates
- 10 8bit Full Adders
- 16 MUX-4 input
- 48 MUX-8 input

Each MUX-2 input has 2 two input AND gate, 1 two input OR gate and 1 NOT gate. Each MUX-4 input has 4 three input AND gate, 1 four input OR gate and 4 NOT gate. Each MUX-8 input has 24 two input AND gate, 7 two input OR gate and 12 NOT gate.

There were several cases where a bus-input MUX (8 inputs of 16 wires, each wire of an input having same hardware to get the output) would have saved the number of MUX.


3 Hardware

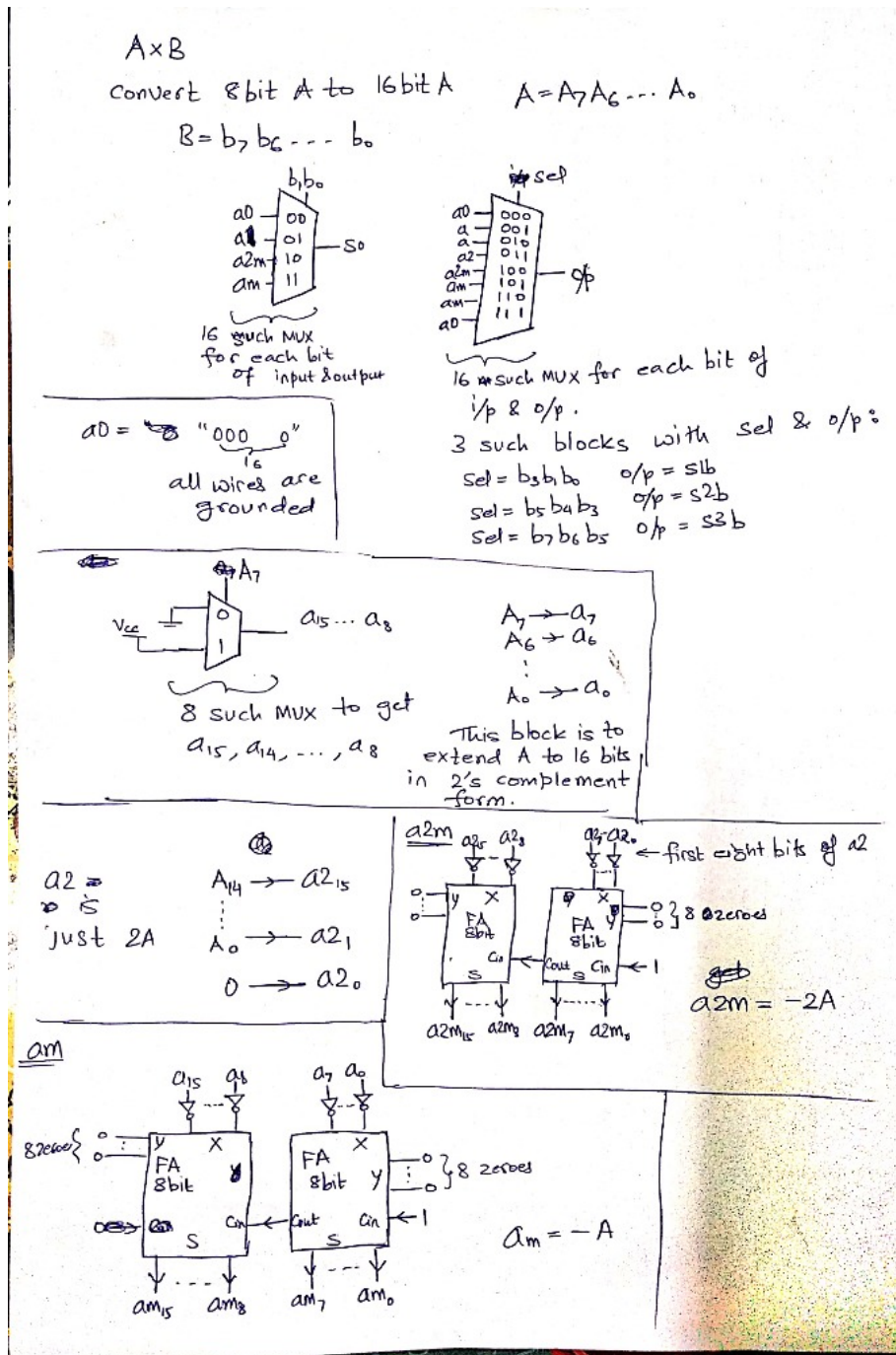

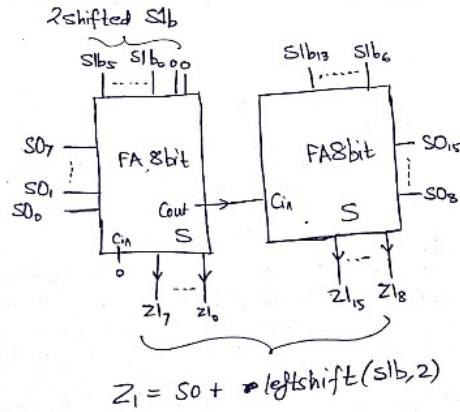  

4 Results

I generated a tracefile that covers all possible inputs and did RTL simulation. It passed all cases and output is shown. It indeed multiplies inputs very fast as seen in Gate level simulation.

```
 Transcript
# Start time: 12:25:19 on Apr 18,2019
# Loading std.standard
# Loading std.textio(body)
# Loading ieee.std_logic_1164(body)
# Loading work.testbench(behave)
# Loading work.dut(dutwrap)
# Loading ieee.numeric_std(body)
# Loading work.booth(struct)
# Loading work.mux_2(str)
# Loading work.fa8bit(fa8bit_beh)
# Loading work.falbit(falbit_beh)
# Loading work.mux_4(str4)
# Loading work.mux_8(str8)
#
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.struct
# view signals
# .main_pane.objects.interior.cs.body.tree
# run -all
# ** Note: SUCCESS, all tests passed.
#   Time: 10485760 ns  Iteration: 0  Instance: /testbench
#
# stdin: <EOF>
```

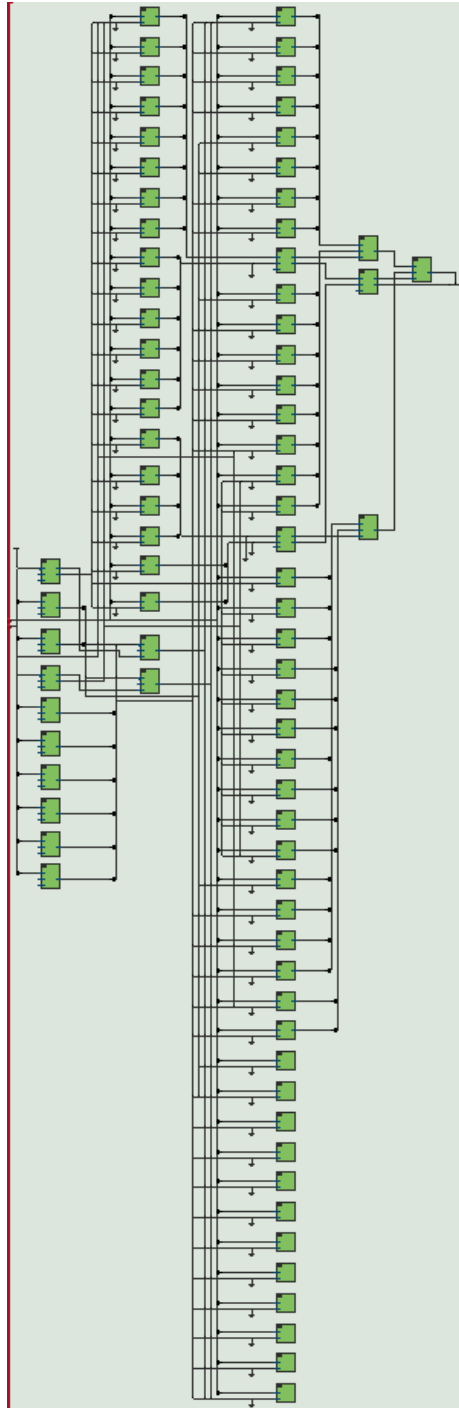


Figure 1: Netlist View